

APPLICABILITY TABLE

| PRODUCTS |
|------------------|
| UE910-EU V2 |
| UE910-NA V2 |
| UE910-EU V2 AUTO |
| CE910-DUAL |
| CE910-SC |



Contents

| | |
|----------------------------------------------|-----------|
| APPLICABILITY TABLE | 2 |
| 1. Introduction | 9 |
| 1.1. Scope | 9 |
| 1.2. Audience..... | 9 |
| 1.3. Contact Information, Support..... | 9 |
| 1.4. Document Organization | 10 |
| 1.5. Text Conventions | 10 |
| 1.6. Related Documents | 11 |
| 1.7. Document History | 11 |
| 2. The Audio Interface | 12 |
| 2.1. Introduction | 12 |
| 2.2. Functional Overview | 12 |
| 3. Why HS, MT and HF | 15 |
| 3.1. Terminology | 15 |
| 3.2. Introduction | 18 |
| 3.2.1. History..... | 18 |
| 3.2.2. Nowadays transducers..... | 18 |
| 3.3. Selection mode | 19 |
| 4. Electrical Characteristics | 20 |
| 4.1. Input lines | 20 |
| 4.2. Output lines | 21 |
| 5. Single Ended or Differential | 22 |
| 5.1. Concepts | 22 |
| 5.1.1. Advantages..... | 22 |
| 5.1.2. Disadvantages | 23 |
| 6. Microphone Amplifier | 24 |
| 6.1. Single Ended (unbalanced)..... | 24 |
| 6.2. Differential (balanced) | 24 |
| 6.3. Suggestions..... | 25 |
| 6.3.1. EMI protection | 25 |



- 7. Speaker amplifier26**
 - 7.1. Single Ended (S.E.) 26
 - 7.2. Differential (BTL) 26
 - 7.3. Suggestions..... 27
- 8. Electret Microphone.....28**
 - 8.1. Generality 28
 - 8.2. Principle of operation 28
 - 8.3. Types 28
 - 8.4. Performance 29
 - 8.4.1. Electrical Characteristics..... 29
 - 8.4.2. Differential Connection Advantages..... 30
 - 8.4.3. Internal Amplifier 30
 - 8.5. Biasing Voltage 30
 - 8.5.1. Biasing Source 31
 - 8.5.2. Reminder..... 31
 - 8.5.3. Unbalanced Biasing 32
 - 8.5.4. Practical Suggestions 32
 - 8.5.5. Balanced Biasing..... 33
 - 8.5.5.1. Suggestions 33**
- 9. Input Paths Guide Lines35**
 - 9.1. Reminder 35
 - 9.2. Noise immunity 35
 - 9.3. Practical suggestions 36
 - 9.3.1. Hands Free 37
 - 9.4. Definitions..... 37
 - 9.4.1. Normal Spoken Condition 37
 - 9.4.2. Sensitivity and electrical equivalent level..... 37
 - 9.4.3. Microphone Electrical Level..... 38
 - 9.5. Microphone connections 38
 - 9.5.1. Coupling..... 38
 - 9.5.1.1. Practical Suggestions 39**
 - 9.5.1.2. Losses Compensation..... 39**
 - 9.5.2. Maximum Gain 40
 - 9.5.2.1. With External Amplifier 40**
 - 9.5.2.2. Without External Amplifier 40**



1.4. Document Organization

This document contains the following chapters:

[Chapter 1: “Introduction”](#) provides a scope for this document, target audience, contact and support information, and text conventions.

[Chapter 2: “The Audio Interface”](#) gives a functional overview of the Audio Interface.

[Chapter 3: “Why HS, MT and HF”](#) tries to give an explanation from an historical point of view about the fundamental differences between these acronyms.

[Chapter 4: “Electrical Characteristics”](#) describes the equipment providing considerations about the input and output lines of the equipment.

[Chapter 5: “Single Ended or Differential”](#) provides a discussion about the use of these configurations.

[Chapter 6: “Microphone Amplifier”](#) provides a discussion about the use of the available configurations when designing microphone amplifiers.

[Chapter 7: “Speaker amplifier”](#) provides a discussion about the use of the available configurations when designing speaker amplifiers.

[Chapter 8: “Electret Microphone”](#) provides a technical description and considerations about electrets microphones (ECM).

[Chapter 9: “Input Paths Guide Lines”](#) indicates the Differential one as a better configuration choice and provides practical suggestions.

[Chapter 10: “Output paths guidelines”](#) indicates the Differential one as a better configuration choice and provides practical suggestions.

[Chapter 11: “Echo cancellation”](#) explains how to overcome the acoustic echo signal disturbance implementing an Acoustic Echo Controller in the firmware of the baseband chip.

[Chapter 12: “Safety Reccomendations”](#)

1.5. Text Conventions



Danger – This information MUST be followed or catastrophic equipment failure or bodily injury may occur.



Caution or Warning – Alerts the user to important points about integrating the module, if these points are not followed, the module and end user equipment may fail or malfunction.



Tip or Information – Provides advice and suggestions that may be useful when integrating the module.

All dates are in ISO 8601 format, i.e. YYYY-MM-DD.



2. The Audio Interface

2.1. Introduction

The Audio Interface is one part of the Baseband System. It comprises the digital and analog circuits for receive and transmit audio operation and ringing.

In this document only the analog blocks will be dealt with, but at its end you can find some paragraphs that describe the functionalities and suggest the implementations of the Echo Canceller/Noise Suppressor modules that allow the use of the Telit modules in Handsfree or Car kit environments, even if they are digital parts of the firmware section.

In the rest of the document we shall refer to *Baseband Audio Interface*.

2.2. Functional Overview

The *Audio Interface* can be considered organized in three sections:

- Interface to processor cores
- Digital filters
- Analog circuits

As declared, in this document we shall describe only the analog circuits that transform the signals to and from the digital part of Baseband chip into analog signals usable by both receive (*Downlink*) and transmit (*Uplink*) audio sections.

The following main functional blocks could be recognized:

- Microphone supply generation
- Analog Input filtering and buffering
- Analog Output filtering and buffering
- Ringer generation

The *Audio Interface* has two major operation modes, featuring a high quality DAC/ADC conversion with buffering stages, allowing the connection of external acoustic transducers as shown in figure 1:

- *Power-down mode* . All analog parts are powered down and all digital and analog part clocks are switched off.
- *Audio mode* . All digital filters are connected to the interface buffers and the analog part is enabled.



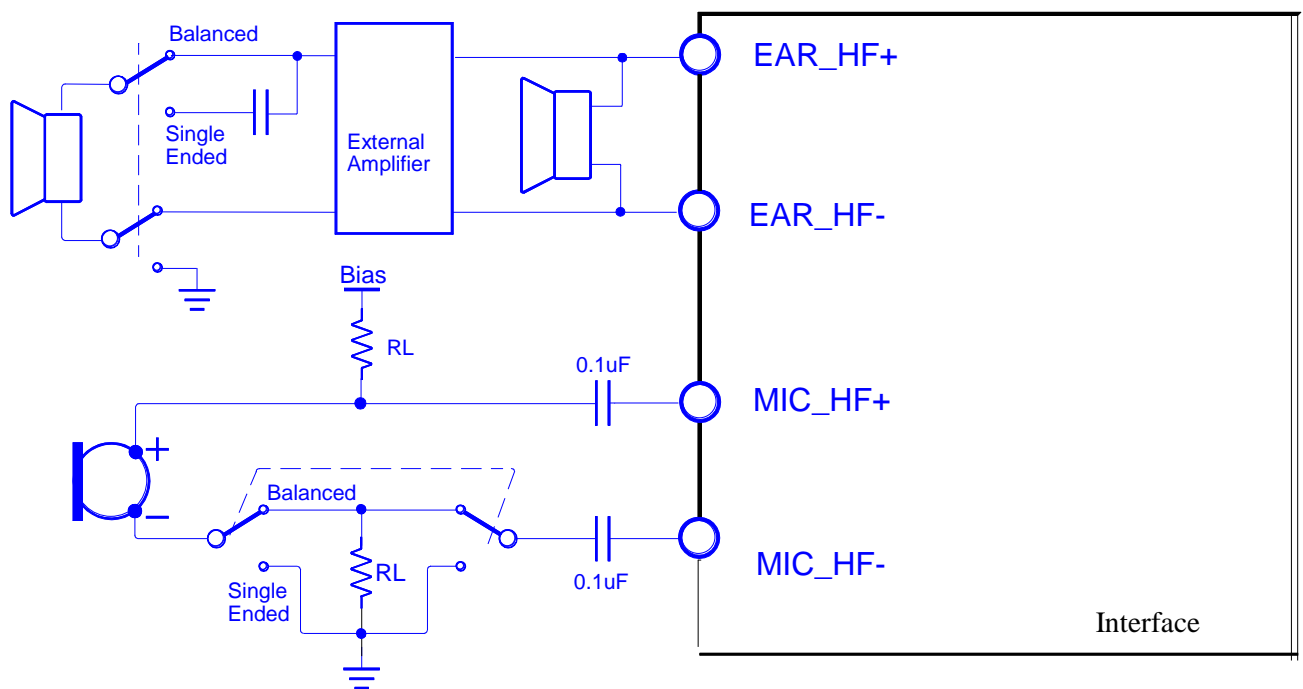


Figure 1. xE910 Available solution to connect external acoustic transducers to *Audio Interface*.





A *Fixed Handsfree* kit fitted in the telephone unit is called **Speakerphone**.

It may be divided into *half-duplex* and *full-duplex* type:

the first one allows sound to travel in one direction at a time (*from the telephone line to its user or from its user to the telephone line*), while the second one is able to transmit and receive simultaneously without discernible change of transmission direction.

← Figure 9. The *Office environment* version

A *Fixed Handsfree* kit fitted into a car is called **CAR-KIT**.

It may be used by the driver and/or the passengers.

It is mandatory its use in the vehicles while driving.



Figure 10. The car environment version. →



3.3. Selection mode

The activation of the requested audio section is made by software by **AT#CAP** command, turning on:

- an output stage to drive a low impedance earpiece and an input stage to drive the handset microphone when in HS/HF mode;
- an output stage to drive a high impedance headset and an input stage to drive the headset microphone when in HF mode.

The *SIDETONE* functionality is on at request in both modes.

Remember that if you don't have any load driving constraint (*like a speaker with an impedance coil lower than 32Ω*), being the performances between the two blocks almost the same, the choice could be done in order to overcome the PCB design difficulties, without considerations to the electrical performances, but respecting the Baseband chip specifications.



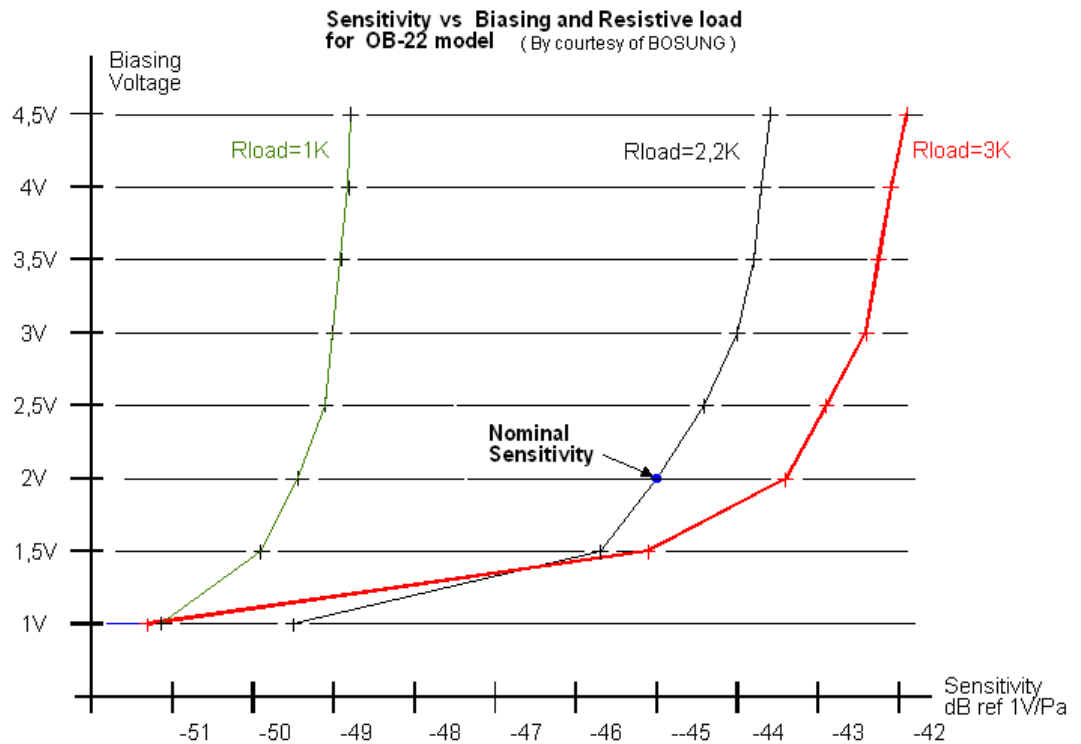


Figure 18. Sensitivity behavior of ECM model OB-22 (By courtesy of BOSUNG)

8.5.1. Biasing Source

The microphone could be powered from the **Audio Interface** itself or from a low noise external source.

Being the microphone circuitry the more noise sensitive, its design and layout must be done with particular care. Both microphone paths have been designed to implement the balanced configuration; if the OEM circuitry is balanced too, then the common mode noise typically generated on the ground plane is reduced.

However some customers strongly request the minus terminal of the microphone grounded and also an unbalanced circuitry can be used for OEM application.

Likewise the amplifiers two different power supply concepts are involved for the biasing:

- unbalanced biasing
- balanced biasing

8.5.2. Reminder

The ECMs have a hot wire were the positive biasing must be connected. Usually it is indicated by a plus (+) symbol or a red point (●). If the polarity of the bias is reversed, then the microphone will not work properly.



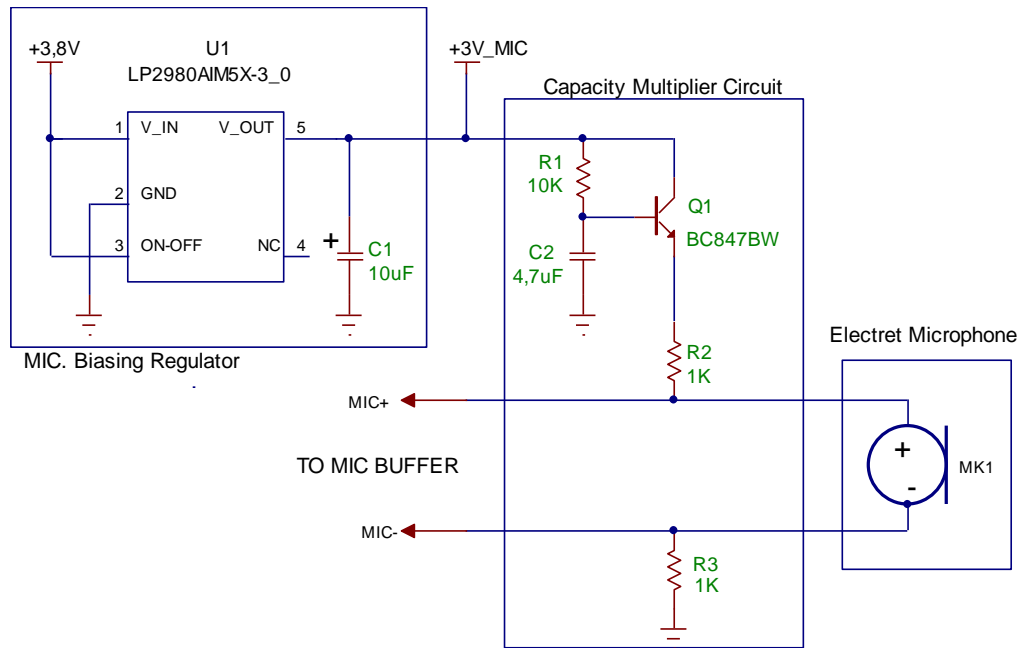


Figure 20. Example of differential microphone biasing supply



9. Input Paths Guide Lines

9.1. Reminder

As discussed at paragraph 4, there are several configurations for the input audio paths, but the best solution is the differential one, that uses 2 tracks to connect the microphone to its amplifier.

It is highly recommended to keep the whole microphone paths balanced.

9.2. Noise immunity

It is very important to have high noise immunity, because the frequency between bursts is 216Hz and falls in audio bandwidth. Because of the RF rectification, the generated disturbance becomes sometimes quite impossible to take off without strong shielding of the audio part of the PCB.

The best microphones contain two small value capacitors inside (*one for 900MHz and the second for 1800-1900MHz band*), which act as RF bypass to short-circuit the RF frequency components to ground, avoiding rectification phenomena.

Not only, the “source” pin is directly connected to its shield, and a lot of ground vias form a sort of shielded case.

When the screening action is not enough, you will hear a sort of noise we call Buzzing, because it seems to be a bug with its buzz sound, whose level depends from TX power.

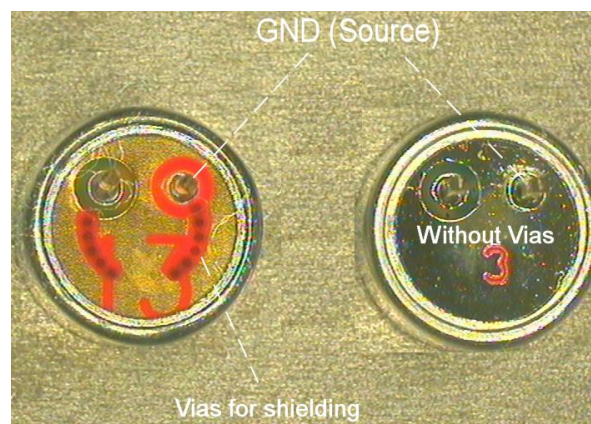


Figure 20 bis. At left the best shielded electret microphone.



9.4.3. Microphone Electrical Level

Knowing the nominal sensitivity of a microphone, it is possible to calculate the voltage level on its pins under “*normal spoken*” condition.

A microphone having the nominal sensitivity of $-45\text{dBV}_{\text{rms}}/\text{Pa}$ will produce an electrical equivalent signal at its pins:

$$\text{Mic Level} = (-45) + (-4.7) = -49.7 \text{ dBV}_{\text{rms}} \quad \text{or} \quad \text{Mic Voltage} = 10^{(-49.7/20)} = 3.3 * 10^{-3} \text{ V}_{\text{rms}}$$

9.5. Microphone connections

The microphone could be connected whether directly or through a buffer amplifier to the input lines of the module. In the first case the required gain will be set only in the internal **Audio Interface** amplifier stages; in the second case, the required gain will be split between the external amplifier (G_E) and the internal stages (G_I).

Again the external buffer amplifier can be **fully differential** or **single ended** configured: where possible it is always preferable a **fully differential** configuration (*balanced*). The buffering circuit shall be placed close to the microphone or close to the microphone wire connector.

9.5.1. Coupling

When using microphones with codecs that utilize differential inputs, special attention needs to be paid to the DC bias of the input signals. Since op-amps in differential configuration amplify DC as well as AC signals, bias differences are important. In the case of DC, common mode rejection means DC removal when the DC bias of the differential input signals is the same.

However, a mismatch in bias levels can quickly lead to reduce dynamic range since the output bias will be affected by the input bias difference.

Luckily, many codecs manufacturers provide amplifier biasing internally.

When internal biasing is used, DC matching is trivial. AC coupling both differential inputs tracks removes DC bias from both tracks, leaving the codec to provide the appropriate bias for best dynamic range. The figure below shows AC coupled differential inputs connection.



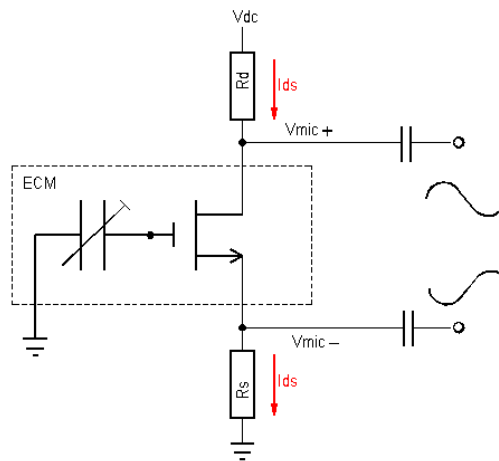


Figure 22. **Fully differential** ECM ac-coupled output signals configuration

9.5.1.1. Practical Suggestions

As previously explained, when the user application is a *handsfree* system, the microphone and the speaker are far from module, driven by external amplifiers. In these environments when designing the external microphone amplifier you must take into account the voice attenuation, due to the distance between the talker and the microphone itself.

You must consider that ambient noise will be picked up.

To overcome these problems, it is preferable to set the gain of the microphone *10dB* lower with respect to the calculated value for a nominal sensitivity. An increased voice volume of the talker, which will speak louder because of the ambient noise, will compensate the corresponding reduction in signal level.

Usually the distance between the microphone and the talker in a *car cabin* is *40/50cm*; in these conditions the attenuation can be considered as a thumb rule around *20dB*.

The same considerations can be made for the *HeadSets* having the microphone on the earpiece cable (like a mobile phone).

The *HeadSets* having the microphone sustained close to the mouth can be threatened as a *HandSet*.

9.5.1.2. Losses Compensation

The voice signal, that in the "*normal spoken*" conditions produces on the microphone membrane an acoustic pressure of *-4,7dBPa* at *1kHz*, will have a further attenuation of *20dB* due the *50cm* distance. A microphone having a sensitivity of *-45dBV_{rms}/Pa* will produce a signal:

$$MicLevel = (-45) + (-4.7) - 20 = -69.7 \text{ dBV}_{rms}$$

equivalent to : $MicVoltage = 10^{(-69.7/20)} = 0,33 * 10^{-3} \text{ V}_{rms}$



If the external amplifier gain $G_E=+10dB$ (3 times), at the *normal spoken* conditions the signal will be:

$$Mic_Input\ Level = 0,33 * 10^{-3} * 3 = 1 * 10^{-3} V_{rms}$$

at the **Audio Interface** input lines , resulting 3 times lower than the nominal as suggested .

These considerations are valid for both **Mic_MT** and **Mic_HF** input lines, if the same configuration is implemented.

9.5.2. Maximum Gain

When you define the gain of the microphone path, keep in mind that the maximum differential level to **Audio Interface** input lines must be $\leq 1,03V_{pp}/-8,67dBV$ (see paragraph 3.1),if the internal gain G_E is set to 0dB.

We have to consider two different configurations: with or without external amplifier.

9.5.2.1. With External Amplifier

Let's calculate the external amplifier gain G_E at strongest voice level condition and internal amplifier gain $G_I=0dB$:

$$\begin{aligned} [(MicLevel + 20dB) + G_E + G_I] &\leq -8,76dBV &\longrightarrow & [-49,7 + 20 + G_E + 0] = -8,76 \\ \text{then } G_E &= (49,7 - 20 - 8,76)dB = +20,94dB &\longrightarrow & G_E = +20dB \quad \text{available by commercial values} \end{aligned}$$

9.5.2.2. Without External Amplifier

Let's calculate the internal amplifier gain G_I at strongest voice level condition and:

$$\begin{aligned} [(MicLevel + 20dB) + G_I] &= -8,76dBV &\longrightarrow & [-49,7 + 20 + G_I] = -8,76 \\ \text{then } G_I &= (49,7 - 20 - 8,76)dB = +20,94dB &\longrightarrow & G_I = +21dB \quad \text{set by dedicated AT command} \end{aligned}$$

9.5.3. Single Ended (Unbalanced) External Amplifier

The next figure shows a possible single ended input microphone amplifier



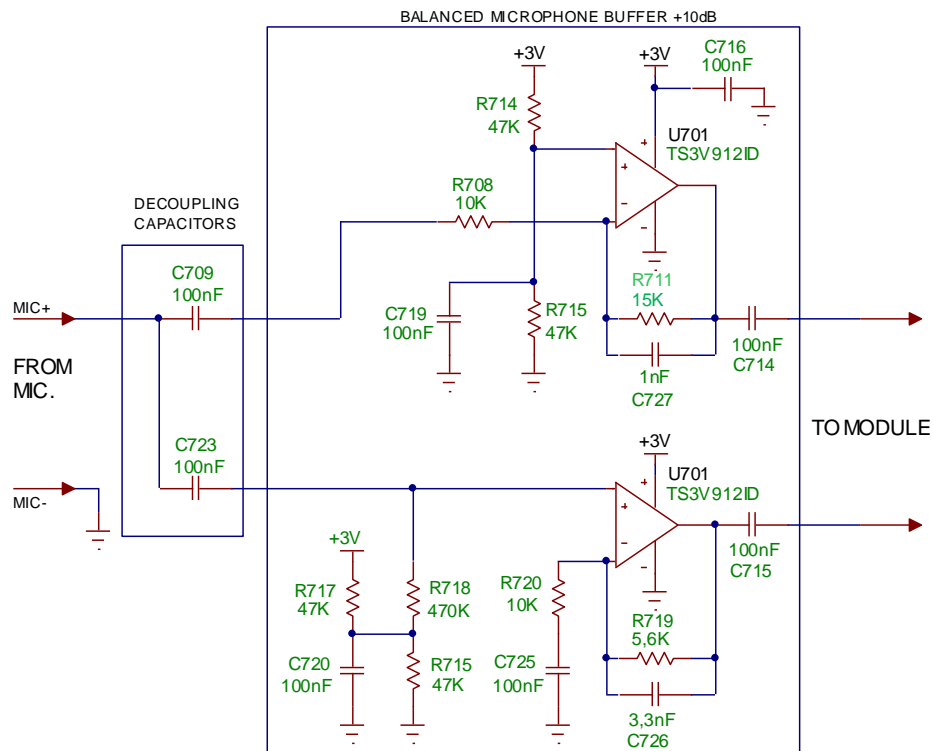


Figure 23. Example of Single ended input microphone amplifier

9.5.3.1. Practical Suggestions

- The gains of the two amplifiers are given by the formulas:

$$Gain(\text{NOT INVERTING BUFFER}) = 1 + \frac{R719}{R720} \quad Gain(\text{INVERTING BUFFER}) = \frac{R711}{R708}$$

Assigning half of overall gain to each amplifier, you will obtain the requested one because of doubling the microphone signal path; in fact by the use of two amplifiers (the upper as “inverting” and the lower as “not inverting” configuration) we obtain an additional +6dB gain (2 times).

Remember: the “not inverting” amplifier section gain shall not be less than 1.

The amplifier overall gain can be modified changing the value of resistor R719/R720/R711, and the capacitors C726/C727 as a consequence.

It is advisable to change R708 **only** if you have difficulty to find a commercial value for R711; in this case change R708 as little as possible because it acts as the input resistance.

- The buffer bandwidth at -3dB shall be 4KHz.
- Considering $C725 \gg C726$, the -3dB bandwidth is given by the approximated formula:

$$freq. = \frac{1}{2\pi * R719 * C726} = \frac{1}{2\pi * R711 * C727} \text{ [Hz]}$$



The commercial values of $15k\Omega$ and $5.6k\Omega$ could be used.

As a consequence of the assigned resistor values, the nominal values of C726 and C727 should be:

$$C726 = 1 / (2\pi * 4000 * R719) = 7.10 * 10^{-9} \text{ F}$$

$$C727 = 1 / (2\pi * 4000 * R711) = 2.65 * 10^{-9} \text{ F}$$

rounded off at $6,8nF$ ($f_{cl}=4181Hz$) and $2,7nF$ ($f_{cu}=3931Hz$) commercial values.

9.5.4. Fully Differential (Balanced) Buffering

The next figure shows a possible fully differential input amplifier.

This circuit has a gain $G_E = 15$ (almost +24 dB) and could be applied both to “Mic_MT” and “Mic_HF” input lines. The gain adjustment shall be done by changing the resistors R604 and R606 and as a consequence the capacitors C636 and C637 to maintain the bandwidth 150-8000Hz (at -3dB).

If the required value for R604 and R606 is not a standard one, you can change R605 and R607 as little as possible because they act as the input resistances.

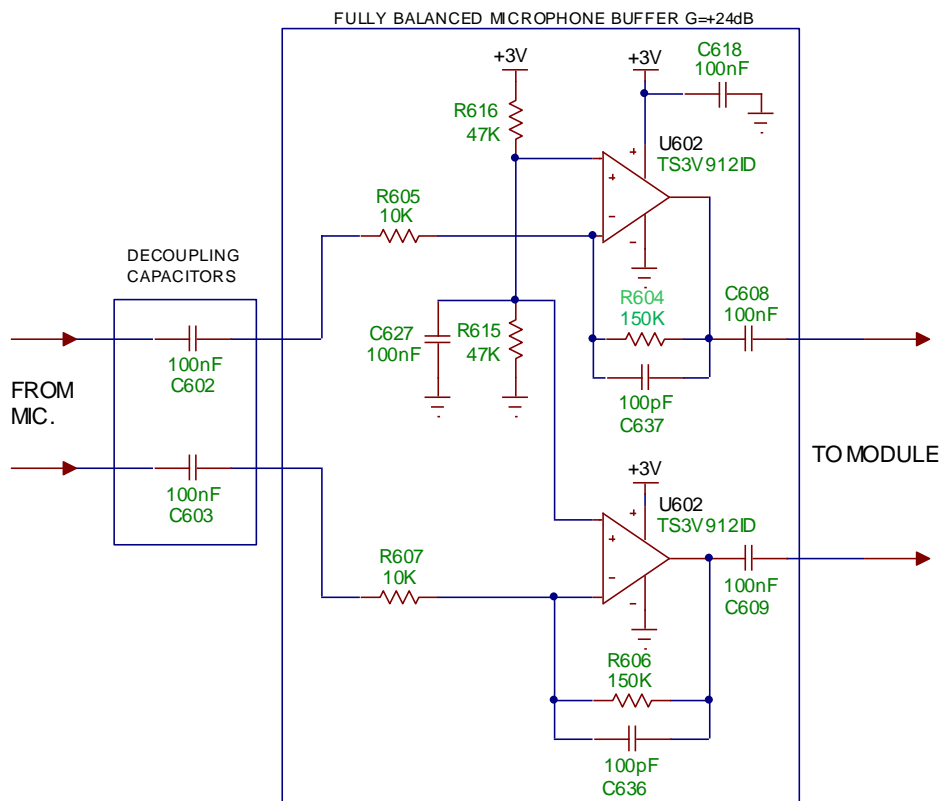


Figure 24. Example of the fully differential microphone amplifier



The buffer gain is given by the formula:

$$Gain = \frac{R604}{R605} = \frac{R606}{R607}$$

The C636 and C637 capacitors are placed in order to cut off the gain at higher frequencies than the transmitted GSM band; the cutoff frequency (-3dB) should be 8000Hz in order to have -1dB at 4KHz.

The cutoff frequency is given by the formula:

$$f_{cu} = \frac{1}{2\pi * R604 * C637} = \frac{1}{2\pi * R606 * C636} \text{ [Hz]}$$

9.5.4.1. Calculus example

Let's assume that:

- you are developing a HandSet application
- you have a microphone with a sensitivity of $-50dBV_{rms}/Pa$ in "normal spoken" conditions at acoustic pressure of $-4.7dBPa$
- you want to use the 1st differential microphone path ("Mic_MT" input lines)
- the buffer amplifier have a gain $G_E=+24dB$ (15 times)
- the desired cutoff frequency of the buffer amplifier is $f_c=4KHz$

The output level from the microphone will be calculated as described in the paragraph 8.4.3:

$$MicLevel = (-50) + (-4.7) = -54.7 dBV_{rms} \text{ or } MicVoltage = 10^{(-54.7/20)} = 1.84 * 10^{-3} V_{rms}$$

When the talker is screaming, the microphone signal will increase by 20dB (10 times) to $18,4mV_{rms}$.

Due to external amplifier, the level at the "Mic_MT" input lines will be:

$$Mic_MT = MicVoltage * G_E = 18,4 * 10^{-3} * 15 = 276mV_{rms}$$

lower enough respect the maximum differential input voltage of $1,03V_{pp}/365mV_{rms}$ as listed at paragraph 3.1 .

Choosing the input resistance $R605 = R607=10k\Omega$, we will obtain the nominal values for the feedback resistors of the buffer:

$$R605 = R607 = G_E * R607 = G_E * R605 = 10 * 15k\Omega = 150k\Omega$$

corresponding to available commercial values .



As a consequence the values of the capacitors $C636$ and $C637$ shall be:

$$C636=C637= 1/(2\pi*4000*R606)= 265 *10^{-12} F$$

A commercial value of $270pF$ gives a cutoff frequency of $3931Hz$, with an error less than 1,8%.

9.5.5. AFE Mic GAIN PARAMETERS

The differential input signal from the microphone passes a low noise amplifier with gain settings ranging from 0 to +42dB. Gains of the input lines can be adjusted separately, so that a maximal degree of flexibility is achieved, by dedicated AT commands described at paragraph 5.6.12

9.5.6. Transmit Block Diagrams

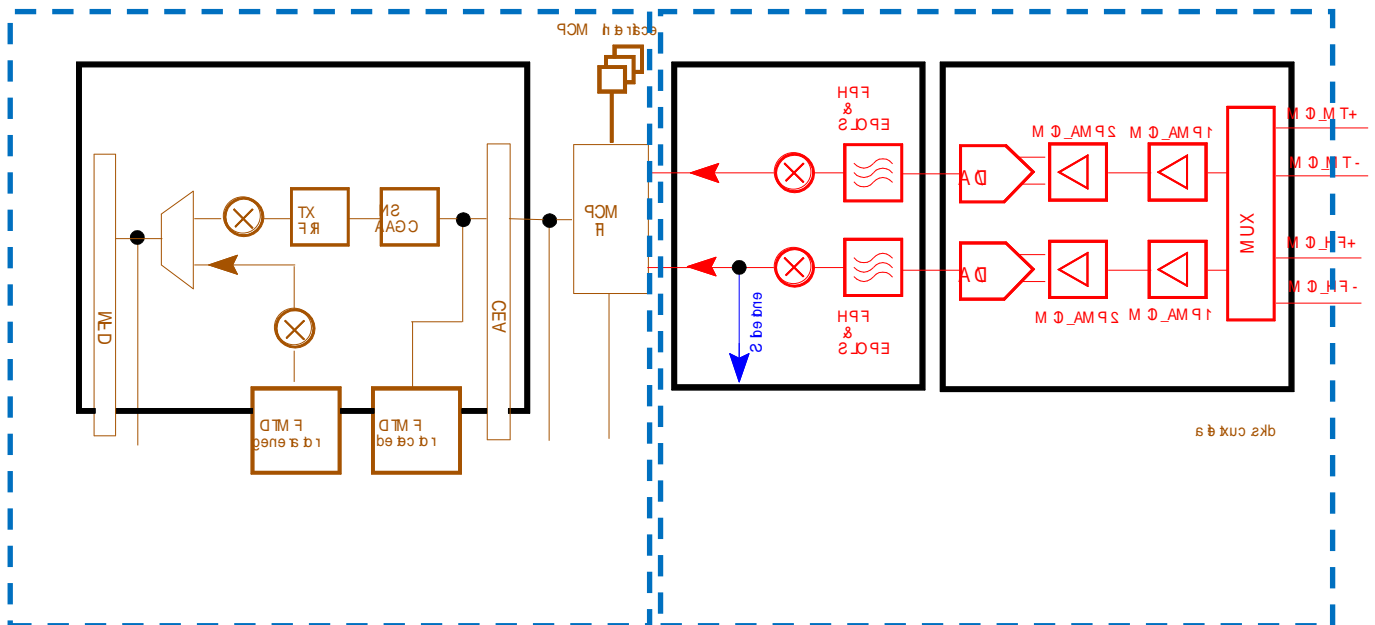


Figure 25 . xE910 Families TX section diagram



10. Output paths guidelines

10.1. Reminder

As suggested at paragraph 4, the differential configuration (*BTL*) is the best implementation for the internal output buffer amplifiers, even if it needs 2 tracks to the load. Obviously, you must respect the electrical characteristics listed at paragraph 4.2.

10.2. Practical suggestions

All the designs shall comply with the following guidelines:

- Where possible use differential configuration (*BTL*) circuitry, to achieve the maximum power output from the device
- Keep the output tracks on the PCB and wires to the transducers as short as possible
- Make sure that the output tracks in the PCB don't cross or run parallel to noisy tracks (especially the power line)
- The cable to the speaker shall be a twisted pair with both the lines floating for the differential output configuration, shielded to ground for the single ended output one.
- If you want to implement a single ended output configuration, that directly drives the load without any external amplifier, leave one of the two output lines open and use only the other referred to ground. Remember that in this case:
 - a) *the output power is 4 times lower than the differential circuit and may not be enough to ensure a good voice volume.*
 - b) *you must use a big decoupling capacitor to the load , and this means more cost and wider PCB .*
- The I/O of the PCB should have a noise filter close to the connector, to filter the high frequency GSM noise. The filter can be a π type formed by an inductor of $39\mu\text{H}$ and 2 capacitors, one of 39pF (0603 case) and the other of 1nF (0603 case)



At low power constraints, you have two possibilities to connect the speaker: directly to module internal buffer amplifiers or through an external amplifier.

The choice will be made considering cost and performance, which generally clash.

At high power constraints, you must use an external power amplifier to boost the module output.

10.5.1. Direct connection

10.5.1.1. HandSets and Portable HandsFree

The direct connection is often the more effective cost solution, reducing the number of components to the minimum. But with some limitations:

- the speaker characteristics has to be almost exactly the suggested ones, otherwise the power output may be reduced (*speaker impedance bigger than 8Ω*) or the output amplification stage may be damaged (*speaker impedance lower than 8Ω*).
- the reduced output power capability may not be enough for some particular applications.

10.5.1.2. Fixed HandsFree

These equipments require greater output:

- speakerphone needs at least 1W
- car kit needs at least 5W

Therefore the direct connection is not allowed.

10.5.2. External Amplifier

10.5.2.1. HandSets and Portable HandsFree

In this case the “*EAR_MT*” or “*EAR_HF*” lines from the *modules* should be AC coupled with a ceramic capacitor of 1uF.

The figure below shows the principle schematic of a differential configuration.



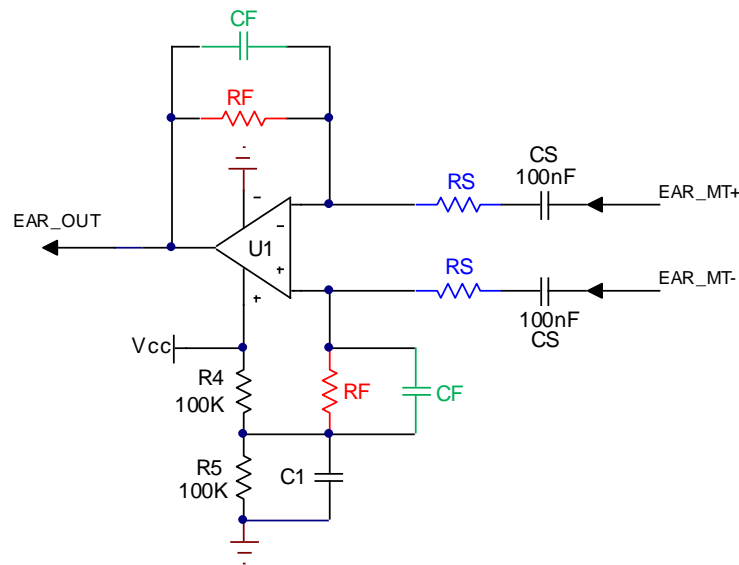


Figure 26. *Differential Output Amplifier* principle schematic

The resulting gain is: $Gain = \frac{RF}{RS}$

With corner frequencies : $f_{cl} = \frac{1}{2\pi * RS * CS}$ [Hz] $f_{cu} = \frac{1}{2\pi * RF * CF}$ [Hz]

Reminding that:

$$X_{C1} = \frac{1}{2\pi * f_{cl} * C1} \text{ and } X_{C1} \ll RF \longrightarrow C1 \geq \frac{1}{2\pi * X_{C1} * f_{cl} * 0.1 * RF}$$

The figures 27 and 28 show the possible schematic of two Audio Power Amplifiers external to **Audio Interface**, that have a mute control (*SHUTDOWN* pin) in order to turn it off while the device is not sending signal to the output; in this way the amplifier background noise is cut off ,avoiding to be audible during idle conditions .

Some amplifiers require a low impedance load at high frequency in order to avoid auto oscillation; this can be made with a capacitor in series with a resistor inserted between output lines and ground (box *Optional* in the figure 27)

When designing your application, remind to provide an adequate bypass capacitor to the amplifier, placing it close to the power input pin of the IC, to have the shortest traces.



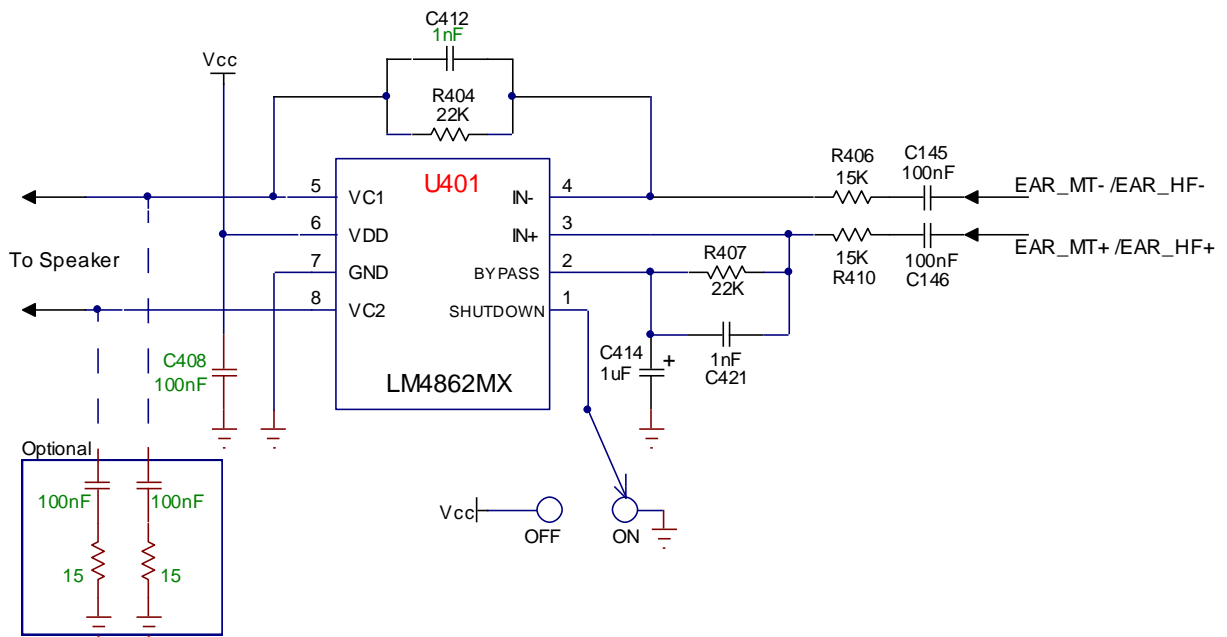


Figure 27. Example of **0.7W** Audio Power Amplifier

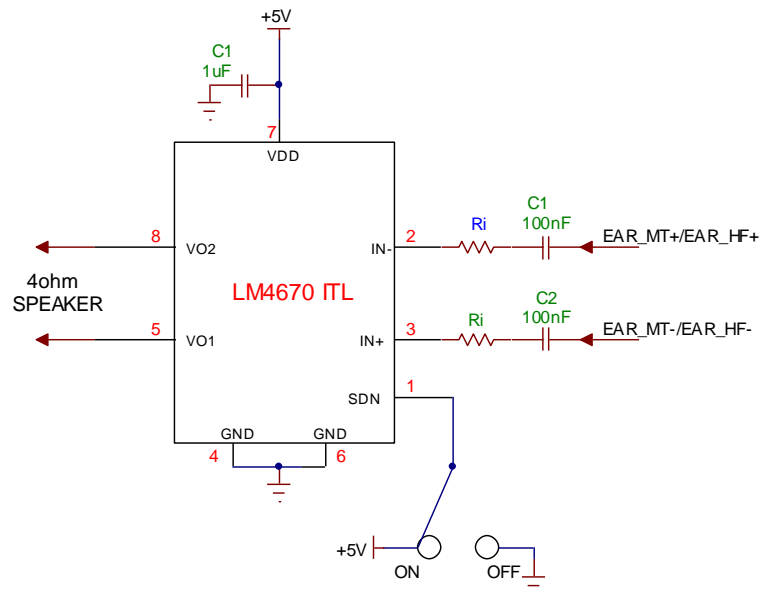


Figure 28. Example of **3W** Audio Power Amplifier



10.6. Audio Interface EAR Gain Parameters

By dedicated AT commands described at paragraph 12.7, the gains of the individual output lines can be adjusted separately so that a maximal degree of flexibility is achieved.

The gain is normalized to **0dBFS** that means $3.7V_{pp}$ /differential and $1,85V_{pp}$ /single-ended.

10.6.1. Receive Block Diagrams

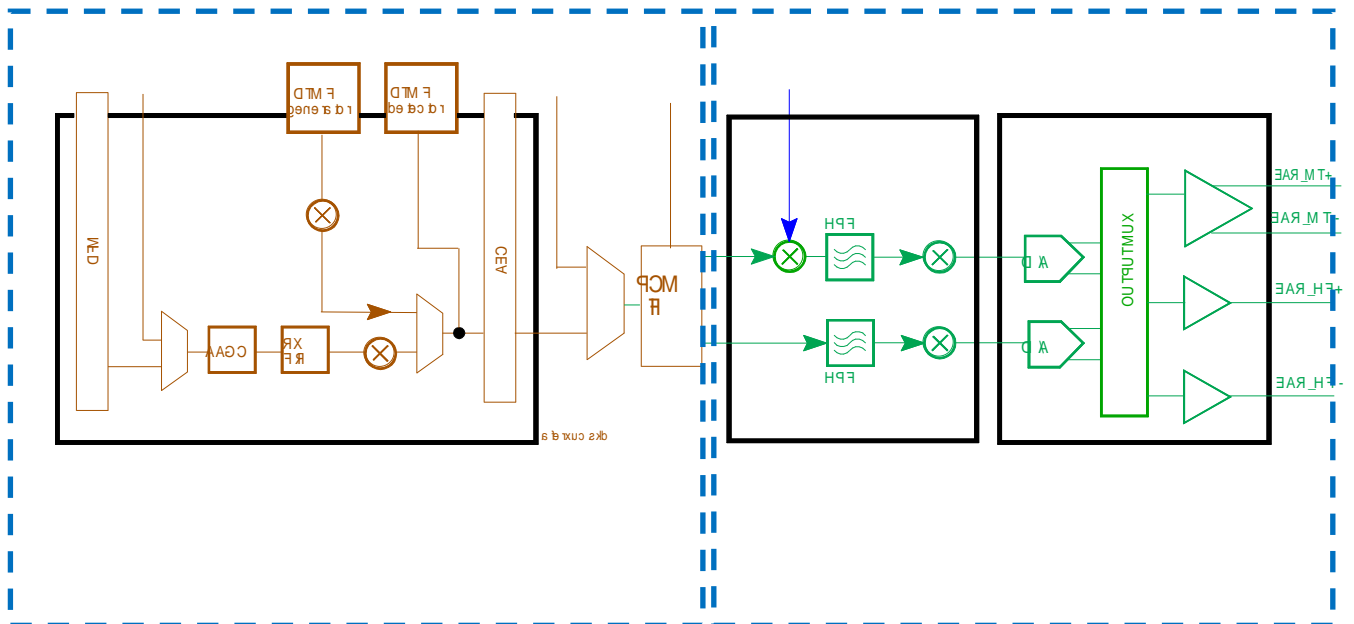


Figure 30. xE910 Families RX section diagram



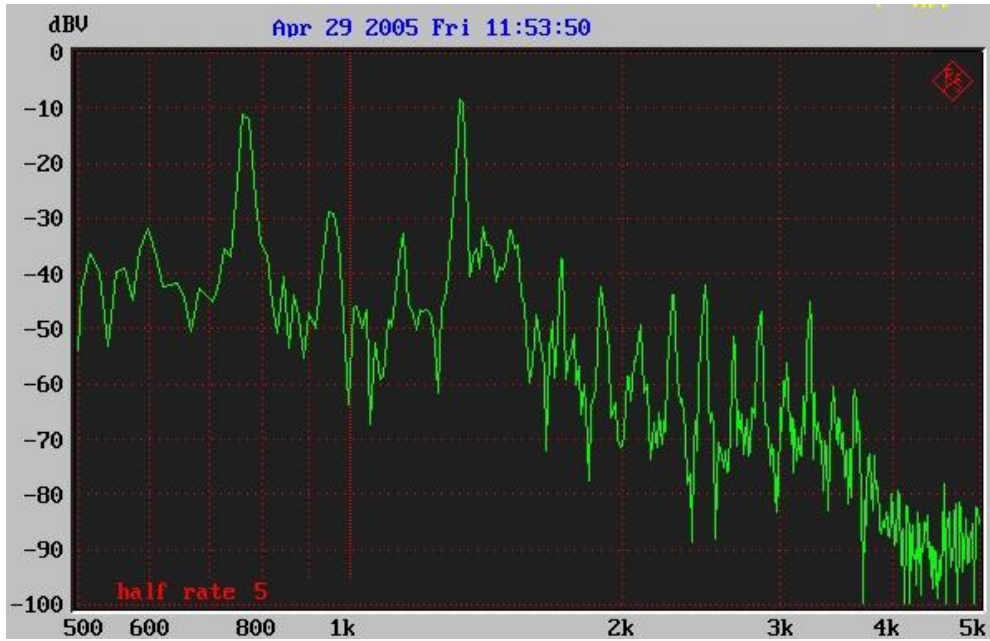


Figure 32. DTMF 5 dialing with *Half Rate* compression type.



Figure 33. DTMF 5 dialing with *Enhanced Full Rate* compression type.



12. Echo cancellation

12.1. Generality

HandsFree systems are equipment that can be used without hands, that is without limiting the movement of the user during a call. They are necessary in several environments:

- in a car's dashboard, while driving
- at the office, during audio or video conferences
- in an elevator, during emergencies
- in open spaces, at the entrance of the parking facilities

These systems are mainly disturbed by the acoustic echo signal that originates from the sound propagation between the loudspeaker and the microphone of a GSM mobile station, sent back to the far user with a significant reduction of the quality.

To overcome this phenomenon, an Acoustic Echo Controller (called *AEC* in the rest of the document) is implemented in the Firmware of the Baseband chip.

12.2. Definition

- *AEC* is voice-operated device used for the purpose of eliminating acoustic echoes and protecting the communication from howling due to acoustic feedback from loudspeaker to microphone.
- *Near-end*: anything related to the local user. E.g.: the *Near-end speaker* is the speaker of the *HandsFree* system in a car
- *Far-end*: anything related to the external user. E.g.: the *Far-end speaker* is the speaker of the *PSTN* user.

12.3. Theory

Acoustic coupling between loudspeaker and microphone is an important and potentially negative feature in phones. A mobile phone will transmit via the microphone the direct signal coming from the near-end speaker, the signal coming from the loudspeaker and noise.

Acoustic echo is formed when the sound emitted by a *HandsFree loudspeaker* gets reflected from the walls, ceilings, floor, furniture, people, etc. back to the *HandsFree microphone*. Sound pressure level decreases with each reflection.



12.5. AEC and Audio parameters AT Commands

The following table lists the AT commands available for audio parameters:

| AT Commands | Description |
|-------------|-------------------------------------|
| AT+CLVL | Loudspeaker Volume Level |
| AT#SHFEC | HandsFree Echo Canceller |
| AT#HFMICG | HandsFree Microphone Gain |
| AT#HSMICG | HandSet Microphone Gain |
| AT#SHFSD | Set HeadSet Sidetone |
| AT#SPKMUT | Speaker Mute Control |
| AT#HFRECG | HandsFree Receiver Gain |
| AT#HSRECG | HandSet Receiver Gain |
| AT#PRST | Audio Profile Factory Configuration |
| AT#PSAV | Audio Profile Configuration Save |
| AT#PSEL | Audio Profile Selection |
| AT#PSET | Audio Profile Settiing |
| AT#SHFNR | HandsFree Noise Reduction |
| AT#SHSEC | HandSet Echo Canceller |
| AT#SHSNR | HandSet Noise Reduction |
| AT#SHSSD | Set HandSet Sidetone |

Note that these commands can be applied only under SELINT=2 AT command interface style.



The commands listed below are example, and may not be supported in a specific Module.

For a detailed description of AT commands please refer to the document AT Commands xE910 - Reference Guide 80419ST10124a and 80399ST1011a.

12.6. Practical Suggestions

In this section, an application example will be described, related to a study of echo cancellation in a silent room environment.



The geometry of the system is a very important aspect of *AEC* parameters tuning, so the first step is to decide the spatially setup of the speaker-microphone system and the setting of the gains (using audio parameters and/or external amplifiers), in order to obtain the right speech levels.

The following figure shows the position of the microphone and speakers as suggested by ITU P.340 Recommendation.

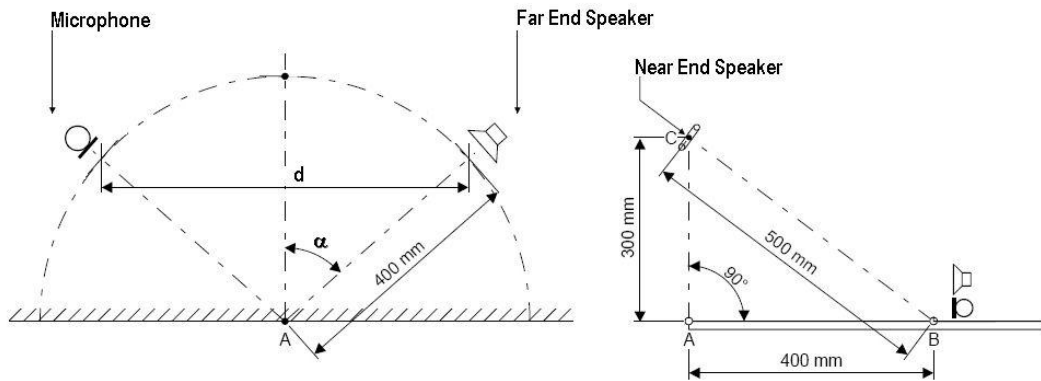


Figure 36. Test setup

We suggest to use an internal microphone gain as low as possible and, if it is needed additional gain to the speaker, to implement it with an external amplifier, using the internal gain only for fine-tuning of the overall downlink gain.



WARNING:

Sidetone is always a harmful effect, so it must be disabled to help echo cancellation action in any HandsFree application.

- Start with the design of the filter length.

The **AEC** has been designed for echo delay $\leq 50\text{ ms}$. For a good cancellation it's enough to take into account only the main echo coming from the near reflections have negligible effects, due to longer delay echoes.

With a distance $d=60\text{cm}$ in our setup we estimated a maximum echo path $L=10\text{m}$, which led to:

$$t = \frac{L}{v_s} = \frac{10\text{m}}{340\frac{\text{m}}{\text{s}}} = 29,4\text{ms} \quad \text{where } v_s = \text{sound velocity}$$

We chose **40ms** to have enough margins for the worst cases.

- Consider the level balance of the system.



- Lower LOSS (because of reduction of the distance between speaker and microphone, or modifying the relative orientation of the two elements) has to be compensated like the case of higher gain.
- Vice versa if the LOSS increases.

When you have adjusted the ***RX*→*TX*** value taking into account either the *EC* matter, either the minimum level for *NEAR END* speaker, then next step is to set *Max AGC* attenuation, dependent on application and increasing with strength of echo (due to spatial position or big gains) .

Additional attenuation is useful because it permits to the user to add a fixed contribution to the final value of gain calculated by *AGC*.

We choose 6dB for *additional attenuation*, 0dB for *minimum attenuation* and 12dB for *maximum attenuation*, because these values are a good compromise between reducing echo and maintaining double-talk quality.

On the other hand it is possible to reproduce a half-duplex behaviour setting:

Maximum attenuation=90dB
Additional attenuation=90dB

so if *AGC* kicks due to *RX*→*TX* threshold (maximum effect at -90dB), it will be at *maximum attenuation*.

Intermediate solutions are very closely related to particular application.

Regarding ***Noise Reduction***, it's important to say that its behaviour and tuning are based on subjective tests.

For *maximum attenuation* typical useful values are between 6dB and 18dB, because bigger values determine very poor speech quality.

When tuning the weights parameters it is important to start with the lower ones and then increase values, keeping a small difference between the two (*at least making them equal*).



13. Telit Evaluation kit

Telit supplies the **EVK2** to assist the designer during his developing project phase to develop his own applications based on present and future GSM/GPRS/WCDMA Telit modules. The **EVK2** provides a fully functional solution for a complete data/phone application, and is formed by a CS1139B motherboard plus several dedicated *Telit modules Interface Boards* with RF antenna connectors, as shown in the figure 39.



Figure 39. *EVK2* (below) with and *GE863-PY* interface (upon).

For further details about **EVK2** and its use in designing audio solutions, please refer to the **Telit EVK2 User Guide (1vv0300704)**.

